

Einführung in die Rechnerarchitektur

Wintersemester 2017/2018

Tutorübung 11: VHDL-Basiskomponenten (Lösungen)

15.01–19.01.2018

VHDL Signale

1. (a)

Signal	A	B	C	D	E	F	G	H	I
Bits	1	1	1	1	8	10	8	8	8

- (b)
- `std_logic_vector` für Bitmuster, Bits können alle Werte von `std_logic` annehmen, neben 0 und 1 z.B. auch undefiniert (U) (weitere: X, L, H, Z, W)
 - `unsigned` für vorzeichenlose Zahlen
 - `signed` für vorzeichenbehaftete Zahlen
 - Zuweisung, Rechnen und Vergleich mit Integerzahlen nur bei `unsigned` und `signed` möglich


(c)

```
signal K : std_logic := '1';  
signal L : std_logic_vector(3 downto 0) := "1010";  
signal M : unsigned(2 downto 0) := 7;  
signal N : unsigned(7 downto 0) := x"EA";  
signal O : std_logic_vector(7 downto 0) := (others => 'U');
```

(d)


```
A <= not B;  
B <= '1' when G = "11111111" else '0';  
C <= A or (not B and D); -- Präzedenz beachten:  
-- not bindet stärker, and und or binden gleich stark  
D <= G(0);  
E <= H(5 downto 0) & "00";  
F <= ("00" & H) + (I(7) & I(7) & I);
```

Flip-Flop-Realisierung

 

```
(b) entity rsff is
    port( s      : in  std_logic;
          r      : in  std_logic;
          q      : out std_logic;
          q_not  : out std_logic
        );
end entity;
```
 
```
(c) entity dmsff is
    port( clk     : in  std_logic;
          d       : in  std_logic;
          q       : out std_logic;
          q_not   : out std_logic
        );
end entity;
```



interne Signale: q_intern, q_not_intern, wobei

```
q_not_intern <= not q_intern;
```

```
(e) architecture behaviour of rsff is
    signal q_intern : std_logic;
    signal q_not_intern : std_logic;
begin
    q_intern <= '1' when s = '1' else
                '0' when r = '1' else
                q_intern;

    q_not_intern <= not q_intern;


    q <= q_intern;
    q_not <= q_not_intern;
end architecture;
```

```
(f) architecture behaviour of dmsff is
    signal q_intern : std_logic;
begin
    q <= q_intern;
    q_not <= not q_intern;

    process(clk)
    begin
        if rising_edge(clk) then
            q_intern <= d;
        end if;
    end process;
end architecture;
```

Seriell-Parallel-Wandler

3.

 

4. (a) entity schieberegister is

```
port( CLK : in std_logic;
      S  : in std_logic;
      P  : out std_logic_vector(7 downto 0)
    );
end entity;
```

(b) architecture behaviour of schieberegister is

```
signal p_intern : std_logic_vector(7 downto 0);
begin
  P <= p_intern;

  process(CLK)
  begin
    if rising_edge(CLK) then
      p_intern <= p_intern(6 downto 0) & S;
    end if;
  end process;
end architecture;
```

BCD-Countdown

5. (a) $\lceil \lg(10) \rceil = 4$, also 4 Bits

```
(b) entity COUNTDOWN is
    port(   CLK       : in  std_logic;
           VALUE     : out unsigned(3 downto 0);
           BCD       : out std_logic
    );
end entity;
```

```
(c) architecture v1 of COUNTDOWN is
    signal z : unsigned(3 downto 0);
begin
    BCD <= '1' when z <= 9 else '0';
    VALUE <= z;

    process(CLK)
    begin
        if rising_edge(CLK) then
            z <= z - 1;
        end if;
    end process;
end architecture;
```

6. (a) entity SEVENSEGMENT is

```
    port(   CLK           : in  std_logic;
           VALUE          : in  unsigned(3 downto 0);
           BCD            : in  std_logic;
           SEGMENTS      : out std_logic_vector(6 downto 0)
    );
end entity;
```

(b) architecture v1 of SEVENSEGMENT is

```
    type rom_type is array 0 to 9 of std_logic_vector(6 downto 0);
    signal rom : rom_type;
begin
    process(CLK)
    begin
        if rising_edge(CLK) then
            if BCD = '1' then
                SEGMENTS <= rom(VALUE);
            end if;
        end if;
    end process;
end architecture;
```